

It's All About the Processors  
14:332:439:02 - Embedded Systems Hardware/Software  
Lab 5  
Raphaelle Marcial  
December 04, 2017

## Purpose

This lab involved incorporating components from previous labs in designing and implementing a 16-bit GRISC processor utilizing instructions for video and communications. The instruction set architecture used by this processor somewhat mirrored those used by a general MIPS processor. This lab also introduced working in the IP Integrator since a block design interface was used in order to create the top-level design.

## Prelab

### Theory of Operation

The ALU was modified to perform the corresponding operations in the GRISC instruction set. Along with the traditional arithmetic instructions, this ALU also included instructions for utilizing the UART through the send and rcv instructions. Moreover, the ALU performed operations on the pixels through the wpix and rpix instructions.

The pixel\_pusher entity was modified to display a 64x64 resolution image by adding a vcount signal to the design. Furthermore, a 16-bit pixel signal was divided between the VGA RGB outputs to have 5, 6, and 5 bits respectively.

## Design

### myALU.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity myALU is
port (
    clk, en : in std_logic;
    A : in std_logic_vector(15 downto 0);
    B : in std_logic_vector(15 downto 0);
    Opcode : in std_logic_vector(3 downto 0);
    Y : out std_logic_vector(15 downto 0)
);
end myALU;

architecture Behavioral of myALU is
begin

    process(clk) begin
        if (rising_edge(clk) and en = '1') then
            case Opcode is
                when "0000" => Y<= std_logic_vector(unsigned(A) + unsigned(B));
                when "0001" => Y<= std_logic_vector(unsigned(A) - unsigned(B));
                when "0010" => Y<= std_logic_vector(unsigned(A) sll 1);
                when "0011" => Y<= std_logic_vector(unsigned(A) srl 1);
                when "0100" => Y<= A(15) & A(15 downto 1);
                when "0101" => Y<= A and B;
                when "0110" => Y<= A or B;
                when "0111" => Y<= A xor B;
                when "1000" =>
```

```

if (signed(A) < signed(B)) then
    Y(0) <= '1';
    Y(15 downto 1) <= (others => '0');
else
    Y(15 downto 0) <= (others => '0');
end if;

when "1001" =>

    if (signed(A) > signed(B)) then
        Y(0) <= '1';
        Y(15 downto 1) <= (others => '0');
    else
        Y(15 downto 0) <= (others => '0');
    end if;

when "1010" =>
if signed(A) = signed(B) then
    Y(0) <= '1';
    Y(15 downto 1) <= (others => '0');
else
    Y(15 downto 0) <= (others => '0');
end if;

when "1011" =>
if A < B then
    Y(0) <= '1';
    Y(15 downto 1) <= (others => '0');
else
    Y(15 downto 0) <= (others => '0');
end if;

when "1100" =>
if A > B then
    Y(0) <= '1';
    Y(15 downto 1) <= (others => '0');
else
    Y(15 downto 0) <= (others => '0');
end if;

when "1101" => Y <= std_logic_vector(unsigned(A) + 1);
when "1110" => Y <= std_logic_vector(unsigned(A) - 1);
when "1111" => Y <= std_logic_vector(0 - unsigned(A));

when others => Y <= (others => '0');
end case;
end if;
end process;

```

end Behavioral;

## pixel\_pusher.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity pixel_pusher is
Port (
    clk    : in std_logic;
    en     : in std_logic;
    VS     : in std_logic;
    pixel  : in std_logic_vector(15 downto 0);

```

```

hcount : in std_logic_vector(9 downto 0);
vcount  : in std_logic_vector(9 downto 0);

vid      : in std_logic;
R        : out std_logic_vector(4 downto 0) := (others => '0');
B        : out std_logic_vector(4 downto 0) := (others => '0');
G        : out std_logic_vector(5 downto 0) := (others => '0');
addr     : out std_logic_vector(11 downto 0) := (others => '0')

);
end pixel_pusher;

architecture Behavioral of pixel_pusher is

signal counter : std_logic_vector(11 downto 0);

begin

    addr_count: process(clk)
    begin
        if rising_edge(clk) and en = '1' then

            if VS = '0' then
                counter <= (others => '0');

            elsif vid = '1' and hcount < std_logic_vector(to_unsigned(64, 10)) and vcount < std_logic_vector(to_unsigned(64,
10)) then
                counter <= std_logic_vector( unsigned(counter) + 1 );
                R <= pixel(15 downto 11);
                G <= pixel(10 downto 5);
                B <= pixel(4 downto 0);
            else
                R <= (others => '0');
                G <= (others => '0');
                B <= (others => '0');

            end if;

        end if; --end clock
    end process addr_count;

    addr <= counter;

end Behavioral;

```

## ***Part 1***

### ***Theory of Operation***

This assembly program provided the instructions that were ran through the processor. Two loops were used in this program, the first printed “Hello\_World” over the UART. After this string was printed, the second loop received user-input characters from the UART that were utilized in displaying different colored squares.

### ***Design***

#### **helloWorld.asm**

```
.data
val1: str "Hello_World"

.text

ori $r3 $zero 0
ori $r5 $zero 1
ori $r6 $zero 4095

ori $r8 $zero 0
beg:
// read char, if not zero print it else end
// la $r6 val2
lw $r4 $r3 val1
beq $r4 $zero end
send $r4 //send
add $r3 $r3 $r5 // increment char pointer
j beg

end:
recv $r7
ori $r8 $zero 0
loop:
beq $r8 $r6 end
wpix $r8 $r7
add $r8 $r8 $r5
j loop
```

### ***Simulation***

It worked.

## Part 2

### Theory of Operation

The register entity was created to infer a dual port memory. This memory had both reading and writing capabilities over 32 16-bit words. When designing the memory, an array of 32 indices was used and each index contained a vector of 16 bits. Reading from the memory meant simply assigning the data out signal to its respective register ID. Writing to the memory assigned the input data to the respective register ID. Enables were used so the ports could be used independently.

The framebuffer entity was created to infer a dual port RAM memory. This memory had reading capabilities in both ports and writing in one port over 4096 16-bit words. It was designed similarly as it was an array of 4096 indices where each index contained a 16-bit vector. This entity was different from the ones design so far as there were two clocks utilized. However, they were controlled by the outputs of separate clock divider entities instead of the original clock input.

### Design

#### regs.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity regs is
Port (
    clk, en, reset : in std_logic;
    id1, id2       : in std_logic_vector(4 downto 0); --addresses
    wr_en1, wr_en2 : in std_logic;
    din1, din2     : in std_logic_vector(15 downto 0);
    dout1, dout2   : out std_logic_vector(15 downto 0)
);
end regs;

architecture Behavioral of regs is

    --Memory consisting of 32 16-bit words
    type memory is array (0 to 31) of std_logic_vector(15 downto 0);
    signal registers : memory := (others => (others => '0'));

begin

    dout1 <= registers(to_integer(unsigned(id1)));
    dout2 <= registers(to_integer(unsigned(id2)));

    write : process(clk, reset, en)
    begin

        if reset = '1' then
            registers <= (others => (others => '0'));

        elsif rising_edge(clk) and en = '1' then
            registers(0) <= (others => '0');

            if wr_en1 = '1' then
```

```

        registers(to_integer(unsigned(id1))) <= din1;
    end if;

    if wr_en2 = '1' then
        registers(to_integer(unsigned(id2))) <= din2;
    end if;

end if; --end clock

end process write;

end Behavioral;

```

## framebuffer.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity framebuffer is
Port (
    --clk, en1, en2      : in std_logic;
    clk_a, clk_b         : in std_logic;
    addr1, addr2         : in std_logic_vector(11 downto 0); --addresses
    wr_en1               : in std_logic;
    din1                 : in std_logic_vector(15 downto 0);
    dout1, dout2         : out std_logic_vector(15 downto 0)
);
end framebuffer;

architecture Behavioral of framebuffer is

    --Memory consisting of 4096 16-bit words
    type memory is array (0 to 4095) of std_logic_vector(15 downto 0);
    signal memSignal : memory := (others => (others => '0'));

begin

    -- Port A
    process(clk_a)
    begin
        if(rising_edge(clk_a)) then
            if(wr_en1='1') then
                memSignal(to_integer(unsigned(addr1))) <= din1;
            end if;
            dout1 <= memSignal(to_integer(unsigned(addr1)));
        end if;
    end process;

    --Port B
    process (clk_b)
    begin
        if(rising_edge(clk_b)) then

            dout2 <= memSignal(to_integer(unsigned(addr2)));

        end if;
    end process;

end Behavioral;

```

## Part 3

### Theory of Operation

The controller was a finite state machine that dictated the behavior of each instruction as it was executed in the processor. This behavior basically followed the datapath of a general MIPS processor since the stages involved fetching, decoding, executing, and reading/writing to memory (if applicable). In addition to the usual instructions, there were also states for utilizing the UART and interfacing with pixel data. Some states were broken into multiple clock cycles to account for the latencies in reading from the memory blocks.

### Design

#### controls.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use IEEE.NUMERIC_STD.ALL;

entity controls is port (
-- Timing Signals
clk, en, rst : in std_logic;
-- Register File IO
rID1, rID2 : out std_logic_vector(4 downto 0);
wr_enR1, wr_enR2 : out std_logic;
regrD1, regrD2 : in std_logic_vector(15 downto 0);
regwD1, regwD2 : out std_logic_vector(15 downto 0);
-- Framebuffer IO
fb_wr_en : out std_logic;
--fbRST : out std_logic;
fbAddr1 : out std_logic_vector(11 downto 0);
fbDin1 : in std_logic_vector(15 downto 0);
fbDout1 : out std_logic_vector(15 downto 0);
-- Instruction Memory IO
irAddr : out std_logic_vector(13 downto 0);
irWord : in std_logic_vector(31 downto 0);
-- Data Memory IO
dAddr : out std_logic_vector(14 downto 0);
d_wr_en : out std_logic;
dOut : out std_logic_vector(15 downto 0);
dIn : in std_logic_vector(15 downto 0);
-- ALU IO
aluA, aluB : out std_logic_vector(15 downto 0);
aluOp : out std_logic_vector(3 downto 0);
aluResult : in std_logic_vector(15 downto 0);
-- UART IO
ready, newChar : in std_logic;
send : out std_logic;
charRec : in std_logic_vector(7 downto 0);
charSend : out std_logic_vector(7 downto 0);
);
end controls;

architecture Behavioral of controls is
--Signals
    signal instruct : std_logic_vector(31 downto 0) := (others => '0');
    signal pc      : std_logic_vector(15 downto 0) := (others => '0');
    signal result  : std_logic_vector(15 downto 0) := (others => '0');
```



```

--Rops Signals
signal opcode_r : std_logic_vector(4 downto 0) := (others => '0');
signal source1_r : std_logic_vector(4 downto 0) := (others => '0');
signal source2_r : std_logic_vector(4 downto 0) := (others => '0');
signal dest_r : std_logic_vector(4 downto 0) := (others => '0');

--lops Signals
signal opcode_i : std_logic_vector(4 downto 0) := (others => '0');
signal source_i : std_logic_vector(4 downto 0) := (others => '0');
signal dest_i : std_logic_vector(4 downto 0) := (others => '0');
signal imm_i : std_logic_vector(15 downto 0) := (others => '0');

--Jops Signals
signal opcode_j : std_logic_vector(4 downto 0) := (others => '0');
signal dest_j : std_logic_vector(15 downto 0) := (others => '0');

signal regA, regB, regC : std_logic_vector(15 downto 0);
signal sum : std_logic_vector(15 downto 0);

signal count : std_logic := '0';

--FSM States
type state is (fetch, decode, Rops, lops, Jops, calc, store, jr, recv, rpix, wpix, send_state, equals, nequal, ori, lw,
sw, jmp, jal, finish, getAluResult, getAluResult2, lw2, send_temp); --clrsrc
signal curr : state := fetch;

begin

p: process (clk)
begin

    if rst = '1' then
        --- SET EVERYTHING TO 0
        rID1 <= (others => '0');
        rID2 <= (others => '0');
        wr_enR1 <= '0';
        wr_enR2 <= '0';
        regwD1 <= (others => '0');
        regwD2 <= (others => '0');
        --fbRST <= '0';
        fbAddr1 <= (others => '0');
        fbDout1 <= (others => '0');
        irAddr <= (others => '0');
        dAddr <= (others => '0');
        d_wr_en <= '0';
        aluA <= (others => '0');
        aluB <= (others => '0');
        aluOp <= (others => '0');
        send <= '0';
        charSend <= (others => '0');

        instruct <= (others => '0');
        pc <= (others => '0');
        result <= (others => '0');
        opcode_r <= (others => '0');
        source1_r <= (others => '0');
        source2_r <= (others => '0');
        dest_r <= (others => '0');
        opcode_i <= (others => '0');
        source_i <= (others => '0');

```

```

dest_i <= (others => '0');
imm_i <= (others => '0');
opcode_j <= (others => '0');
dest_j <= (others => '0');
regA <= (others => '0');
regB <= (others => '0');
regC <= (others => '0');
sum <= (others => '0');

curr <= fetch;

elsif rising_edge(clk) and en = '1' then

    case curr is
        --Fetch
        when fetch =>
            if count = '0' then
                rID1 <= "00001";
                curr <= fetch;
                count <= '1';

            else
                pc <= regrD1;
                irAddr <= regrD1(13 downto 0);
                report integer'image(to_integer(unsigned(pc)));
                --NS
                curr <= decode;

            count <= '0';
        end if;

        --Decode
        when decode =>

            if count = '0' then
                instruct <= irWord;

                curr <= decode;
                count <= '1';
            else
                --increment
                rID1 <= "00001";
                regwD1 <= std_logic_vector( unsigned(pc) + 1 );

                wr_enR1 <= '1';

                --NS
                count <= '0';
                if instruct(31 downto 30) = "00" or instruct(31 downto 30) = "01" then

                    curr <= rops;
                elsif instruct(31 downto 30) = "10" then
                    curr <= iops;
                else
                    curr <= jops;
                end if;
            end if;

            --Rops
            when rops =>
                wr_enR1 <= '0';

```

```

opcode_r  <= instruct(31 downto 27);
dest_r    <= instruct(26 downto 22);
source1_r <= instruct(21 downto 17);
source2_r <= instruct(16 downto 12);

```

```

rID1 <= instruct(21 downto 17);
rID2 <= instruct(16 downto 12);

```

```

regA <= regrD1;
regB <= regrD2;

```

```

--NS
if instruct(31 downto 27) = "01101" then
    curr <= jr;
elsif instruct(31 downto 27) = "01100" then
    curr <= recv;
elsif instruct(31 downto 27) = "01111" then
    curr <= rpix;
elsif instruct(31 downto 27) = "01110" then
    curr <= wpix;
    rID2 <= instruct(26 downto 22);
elsif instruct(31 downto 27) = "01011" then
    curr <= send_state;
else
    curr <= calc;
end if;

```

```

--lops
when iops =>
    wr_enR1 <= '0';
    opcode_i  <= instruct(31 downto 27);
    dest_i    <= instruct(26 downto 22);
    source_i  <= instruct(21 downto 17);
    imm_i     <= instruct(16 downto 1);

```

```

rID1 <= instruct(26 downto 22);
rID2 <= instruct(21 downto 17);

```

```

regA <= regrD1;
regB <= regrD2;

```

```

if instruct(29 downto 27) = "000" then
    curr <= equals;
elsif instruct(29 downto 27) = "001" then
    curr <= nequal;
elsif instruct(29 downto 27) = "010" then
    curr <= ori;
elsif instruct(29 downto 27) = "011" then
    curr <= lw;
else
    curr <= sw;
end if;

```

```

--Jops
when jops =>
    wr_enR1 <= '0';
    opcode_j <= instruct(31 downto 27);

```

```

dest_j <= instruct(26 downto 11);

--rID1 <= instruct(26 downto 11);
--regC <= regRD1;

--NS
if instruct(31 downto 27) = "11000" then
    curr <= jmp;
elsif instruct(31 downto 27) = "11001" then
    curr <= jal;
else
    curr <= finish;
end if;

--calc
when calc =>

    aluOp <= opcode_r(3 downto 0);
    aluA <= regrD1;
    aluB <= regrD2;
    curr <= getAluResult;

    when getAluResult =>

        --result <= aluResult;
        curr <= getAluResult2;

        when getAluResult2 =>

            result <= aluResult;
            curr <= store;

            --store

            when store =>
                if count = '0' then
                    rID1 <= instruct(26 downto 22);

regwD1 <= result;

                    wr_enR1 <= '1';
                    count <= '1';
                    curr <= store;
                else
                    wr_enR1 <= '0';
                    count <= '0';
                    --NS
                    curr <= finish;
                end if;
            --jr
            when jr =>
                --rID1 <= dest_j;
                --result <= regRD1;
                result <= dest_j;
                --NS
                curr <= store;

            --recv
            when recv =>
                result <= "00000000" & charRec;
                --NS
                if newChar = '0' then

```

```

        curr <= recv;
    else
        curr <= store;
    end if;

--rpix
when rpix =>
    --rID2 <= instruct(21 downto 17);
    --fbAddr1 <= regrD2(11 downto 0);
    fbAddr1 <= regrD2(11 downto 0);

    result <= fbDin1;

--NS
curr <= store;

--wpix
when wpix =>
    if count = '0' then

        fbAddr1 <= regrD2(11 downto 0);
        --fbAddr1 <= regA(11 downto 0);

        count <= '1';
        curr <= wpix;
    else
        fb_wr_en <= '1';
rID1 <= instruct(21 downto 17);
fbDout1 <= regrD1;

        count <= '0';
        --NS
        curr <= finish;
    end if;
--send
when send_state =>

    if count = '0' then

        rID1 <= dest_r;

        count <= '1';
        curr <= send_state;
    else

        --NS
        send <= '1';
        charSend <= regrD1(7 downto 0);
        --send <= '1';
        count <= '0';
        curr <= send_temp;
    end if;

    when send_temp =>
        send <= '0';
        if ready = '1' then

            curr <= finish;
            count <= '0';

        else
            count <= '0';

```

```
curr <= send_temp;  
end if;
```

```
--equals  
when equals =>  
  if regRD1 = regRD2 then  
    result <= instruct(16 downto 1);  
    instruct(26 downto 22) <= "00001";  
    curr <= store;  
    --dest_i <= regrD1;  
  else  
    curr <= finish;  
  end if;
```

```
--nequal  
when nequal =>  
  if regRD1 /= regRD2 then  
    result <= imm_i;  
    dest_i <= "00001";  
    curr <= store;  
  else  
    curr <= finish;  
  end if;
```

```
--NS
```

```
--ori  
when ori =>
```

```
  result <= regB OR imm_i;  
  --NS  
  curr <= store;
```

```
--lw  
when lw =>  
  if count = '0' then  
    sum <= std_logic_vector( unsigned(regrD2) + unsigned(imm_i) );  
    count <= '1';  
    curr <= lw;
```

```
  else  
    dAddr <= sum(14 downto 0);
```

```
  --NS  
  curr <= lw2;  
  count <= '0';  
  end if;
```

```
when lw2 =>
```

```
  result <= dIn;  
  curr <= store;
```

```
--SW  
when sw =>  
  if count = '0' then  
    sum <= std_logic_vector( unsigned(regrD2) + unsigned(imm_i) );  
    dAddr <= sum(14 downto 0);
```

```

--dOut <= std_logic_vector( unsigned(regB) + unsigned(imm_i) );
    d_wr_en <= '1';
    rID1 <= dest_i;
    dout <= regrD1;
    count <= '1';
    curr <= sw;
else
    d_wr_en <= '0';
    count <= '0';
--dAddr <= regrD1;
--NS
    curr <= finish;
end if;

--jmp
when jmp =>
    if count = '0' then

rID1 <= "00001";
count <= '1';
curr <= jmp;
wr_enR1 <= '1';
regWD1 <= instruct(26 downto 11);
else

    wr_enR1 <= '0';
    count <= '0';

--NS
    curr <= finish;
end if;
--jal
when jal =>
    if count = '0' then
        rID1 <= "00001"; --pc
        rID2 <= "00010"; --ra
        wr_enR1 <= '1';
        wr_enR2 <= '1';

        regWD2 <= pc;
        regWD1 <= regC;
        count <= '1';
        curr <= jal;
    else
        --wr_enR1 <= '0';

        count <= '0';
--NS
        curr <= finish;
    end if;

--clrscr
when clrscr =>
    fbRST <= '1';
--NS
    curr <= finish;

--finish

when finish =>
    fbRST <= '0';

```

```

d_wr_en <= '0';
wr_enR1 <= '0';
wr_enR2 <= '0';
count <= '0';
fb_wr_en <= '0';
    curr <= fetch;
when others =>
    curr <= fetch;

```

```

end case;

```

```

end if;

```

```

end process p;

```

```

end Behavioral;

```

## Simulation

 


Figure 1: Waveform of “add \$r3 \$r4 \$r5”



## Part 4

### Theory of Operation

The top-level design combined all the components in the aforementioned parts along with entities used in previous labs to create the processor. Unlike previous labs, a graphical tool was utilized in order to simplify the process of connecting the entities. The inputs for this design were the clock, the txd port of the pmod, and a button that reset the registers, signals in the controllers, and the contents of the UART. The outputs were the vga display signals and the rxd port of the pmod. As soon as the FPGA was programmed, the string "Hello\_World" was displayed on the termite terminal. Furthermore, the characters inputted via the terminal were used in displaying different colored squares.

### Design

#### debounce.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity debounce is
port (
    clk : in std_logic;
    btn : in std_logic;
    dbnc : out std_logic
);
end debounce;

architecture Behavioral of debounce is
    signal count : std_logic_vector (21 downto 0) := (others => '0');
    signal sregister : std_logic_vector (1 downto 0) := (others => '0');

begin
    process(clk)
    begin

        if rising_edge(clk) then
            sregister(1) <= sregister(0);
            sregister(0) <= btn;

            if count = std_logic_vector(to_unsigned(2500000,22)) then
                dbnc <= '1';
            else
                dbnc <= '0';
            end if;

            if sregister(1) = '1' then
                if count /= std_logic_vector(to_unsigned(2500000,22)) then
                    count <= std_logic_vector(unsigned(count)+ 1);
                end if;
            else
                count <= (others => '0');
            end if;

        end if;

    end process;

end Behavioral;
```

### clock\_1div.vhd (115200 Hz)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity clock_div1 is
port (
    clk : in std_logic;
    div : out std_logic --new clock
);
end clock_div1;

architecture Behavioral of clock_div1 is
    signal count : std_logic_vector (10 downto 0) := (others => '0');
    signal clk_1 : std_logic := '0';
begin

    process(clk)
    begin

        if rising_edge(clk) then

            if count = std_logic_vector(to_unsigned(1084,11)) then
                count <= (others => '0');
                clk_1 <= '1';
            else
                clk_1 <= '0';
                count <= std_logic_vector(unsigned(count) + 1 );
            end if;

        end if;

    end process;

    div <= clk_1;

end Behavioral;
```

### clock\_2div.vhd (25 MHz)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity clock_div2 is
port (
    clk : in std_logic;
    div : out std_logic --new clock
);
end clock_div2;

architecture Behavioral of clock_div2 is
    signal count : std_logic_vector (2 downto 0) := (others => '0');
    signal clk_1 : std_logic := '0';
begin

    process(clk)
    begin

        if rising_edge(clk) then
```

```

    if count = std_logic_vector(to_unsigned(4,3)) then
        count <= (others => '0');
        clk_1 <= '1';
    else
        clk_1 <= '0';
        count <= std_logic_vector( unsigned(count) + 1 );
    end if;

end if;

end process;

div <= clk_1;

end Behavioral;

```

## vga\_ctrl.vhd

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity vga_ctrl is
    Port ( clk : in STD_LOGIC;
          en : in STD_LOGIC;
          hcount : out STD_LOGIC_VECTOR (9 downto 0);
          vcount : out STD_LOGIC_VECTOR (9 downto 0);
          vid : out STD_LOGIC;
          hs : out STD_LOGIC;
          vs : out STD_LOGIC);
end vga_ctrl;

architecture Behavioral of vga_ctrl is
    signal hcount_s : std_logic_vector(9 downto 0) := (others => '0');
    signal vcount_s : std_logic_vector(9 downto 0) := (others => '0');

begin

    incrementing_hcount:process(clk)
    begin

        if rising_edge(clk) then
            if en = '1' then
                if hcount_s = std_logic_vector(to_unsigned(799, 10)) then
                    hcount_s <= (others => '0');
                else
                    hcount_s <= std_logic_vector( unsigned(hcount_s) + 1 );
                end if;
            end if;
        end if;
    end process incrementing_hcount;

    incrementing_vcount:process(clk)
    begin
        if rising_edge(clk) then
            if en = '1' then
                if hcount_s = std_logic_vector(to_unsigned(0, 10)) then
                    if vcount_s = std_logic_vector(to_unsigned(524, 10)) then
                        vcount_s <= (others => '0');
                    else
                        vcount_s <= std_logic_vector( unsigned(vcount_s) + 1 );
                    end if;
                end if;
            end if;
        end if;
    end process incrementing_vcount;
end Behavioral;

```

```

        end if;
    end if;
end process incrementing_vcount;

display:process(hcount_s, vcount_s)
begin
    if hcount_s >= std_logic_vector(to_unsigned(0, 10)) and hcount_s <= std_logic_vector(to_unsigned(639, 10)) and
vcount_s >= std_logic_vector(to_unsigned(0, 10)) and vcount_s <= std_logic_vector(to_unsigned(479, 10)) then
        vid <= '1';
    else
        vid <= '0';
    end if; --end display on/off condition
end process display;

hs_signal:process(hcount_s)
begin
    if hcount_s >= std_logic_vector(to_unsigned(656, 10)) and hcount_s <= std_logic_vector(to_unsigned(751, 10)) then
        hs <= '0';
    else
        hs <= '1';
    end if;
end process hs_signal;

vs_signal:process(vcount_s)
begin
    if vcount_s >= std_logic_vector(to_unsigned(490, 10)) and vcount_s <= std_logic_vector(to_unsigned(491, 10)) then
        vs <= '0';
    else
        vs <= '1';
    end if;
end process vs_signal;

hcount <= hcount_s;
vcount <= vcount_s;
end Behavioral;

```

### uart.vhd (Lab 3 solution)

```

library ieee;
use ieee.std_logic_1164.all;

entity uart is port (
    clk, en, send, rx, rst : in std_logic;
    charSend : in std_logic_vector (7 downto 0);
    ready, tx, newChar : out std_logic;
    charRec : out std_logic_vector (7 downto 0)
);
end uart;

architecture structural of uart is
    component uart_tx port
    (
        clk, en, send, rst : in std_logic;
        char : in std_logic_vector (7 downto 0);
        ready, tx : out std_logic
    );
    end component;

    component uart_rx port

```

```

(
    clk, en, rx, rst : in std_logic;
    newChar : out std_logic;
    char : out std_logic_vector (7 downto 0)
);
    end component;

begin

    r_x: uart_rx port map(
        clk => clk,
        en => en,
        rx => rx,
        rst => rst,
        newChar => newChar,
        char => charRec);

    t_x: uart_tx port map(
        clk => clk,
        en => en,
        send => send,
        rst => rst,
        char => charSend,
        ready => ready,
        tx => tx);

end structural;

```

### tx.vhd (Lab 3 solution)

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity uart_tx is
    Port ( clk : in STD_LOGIC;
          en : in STD_LOGIC;
          send : in STD_LOGIC;
          rst : in STD_LOGIC;
          char : in STD_LOGIC_VECTOR (7 downto 0);
          ready : out STD_LOGIC;
          tx : out STD_LOGIC);
end uart_tx;

architecture Behavioral of uart_tx is

    type state is (idle, data, stop);
    signal curr : state := idle;

    --shift register
    signal d      : std_logic_vector (7 downto 0) := (others => '0');

    --counter
    signal count  : std_logic_vector (2 downto 0) := (others => '0');

begin

    process (clk) begin

        if rst = '1' then

```

```

curr <= idle;
d <= (others => '0');
count <= (others => '0');
tx <= '1';
ready <= '1';

elsif rising_edge(clk) and en = '1' then
  case curr is

    when idle =>
      if send = '1' then
        d <= char;
        ready <= '0';
        count <= (others => '0');
        curr <= data;
        tx <= '0';

      else
        tx <= '1';
        ready <= '1';

      end if;
    when data =>
      tx <= d(0);
      d <= '0' & d(7 downto 1);
      if unsigned(count) < 7 then
        count <= std_logic_vector(unsigned(count) + 1);
      else
        curr <= stop;
      end if;

    when stop =>
      tx <= '1';
      ready <= '0';
      curr <= idle;

    when others =>
      curr <= idle;
  end case;
end if;

end process;
end Behavioral;

```

## rx.vhd (Lab 3 solution)

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity uart_rx is port
(
  clk, en, rx, rst : in std_logic;
  newChar : out std_logic;
  char : out std_logic_vector (7 downto 0)
);
end uart_rx;

architecture fsm of uart_rx is

```







## Simulation

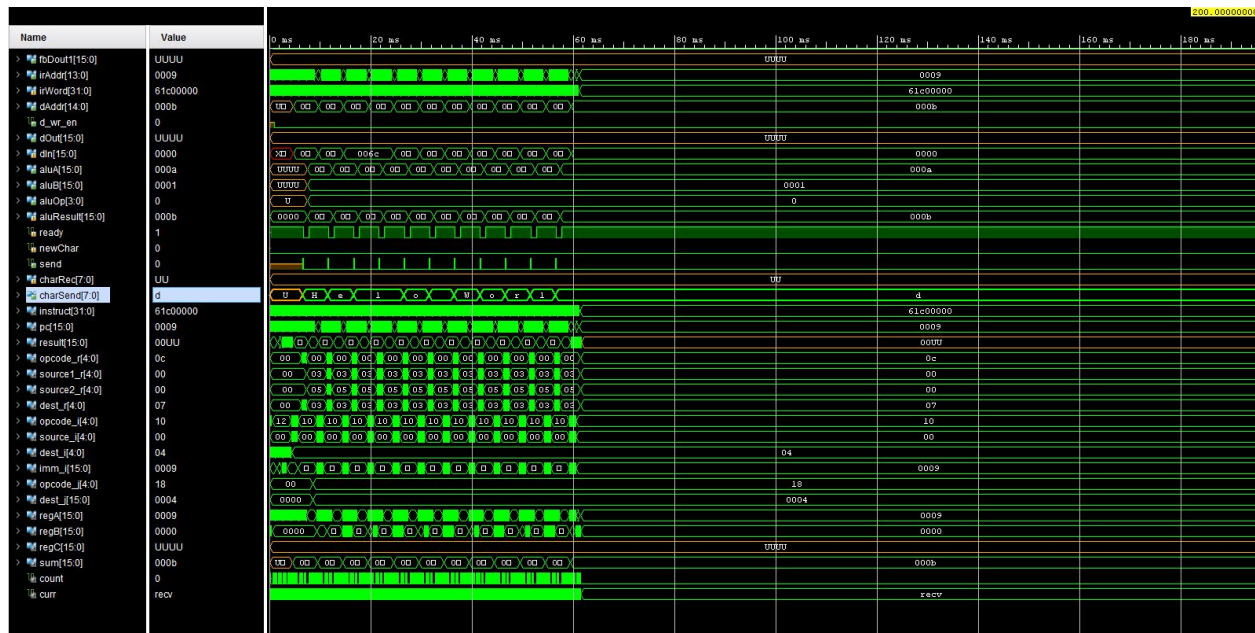


Figure 3: Waveforms when txd = '1' -> Hello\_World



 


Figure 3: Waveforms when txd = '0' -> wpix

### Implementation

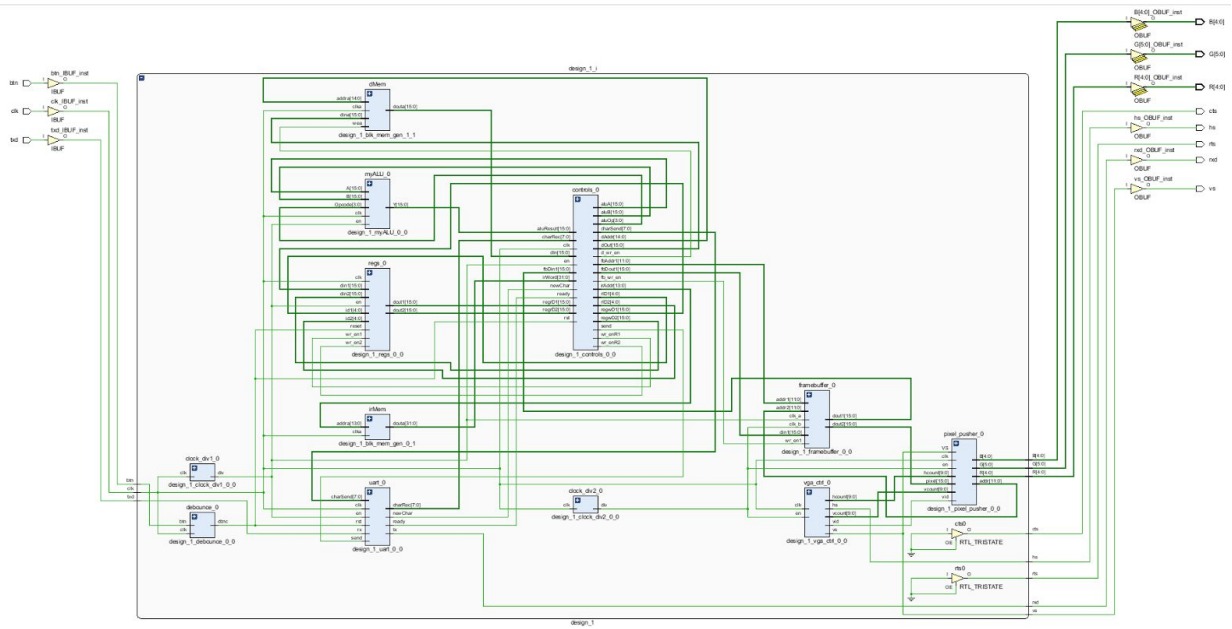

*Figure 4: Elaboration Schematic*

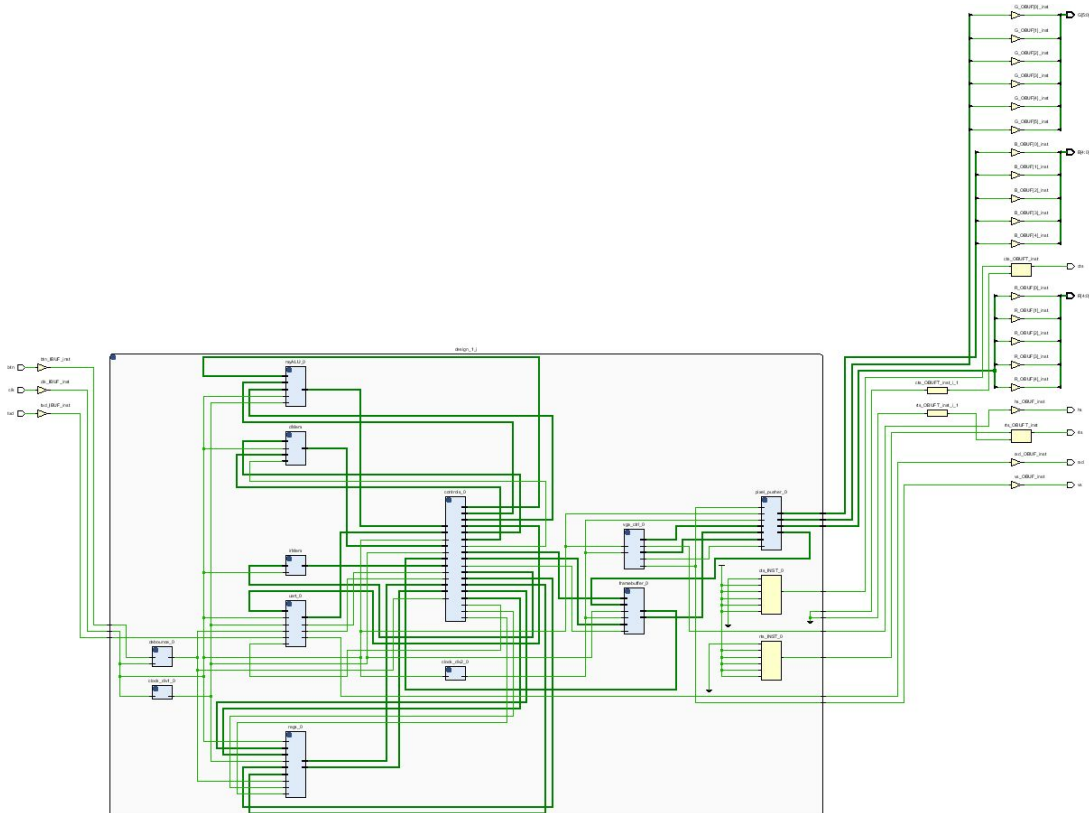

*Figure 5: Full Synthesis Schematic*

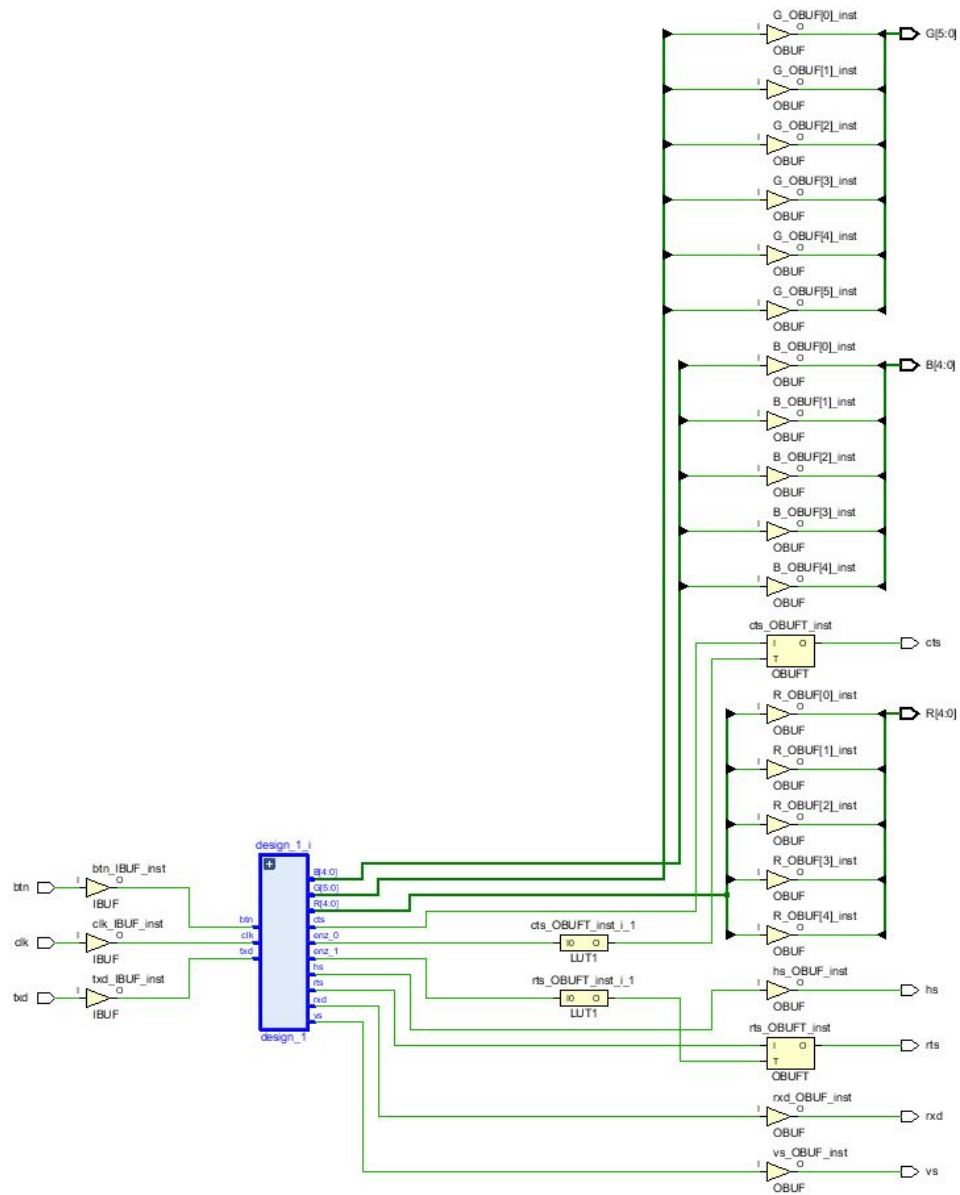


Figure 6: Synthesis Schematic with wrapper minimized

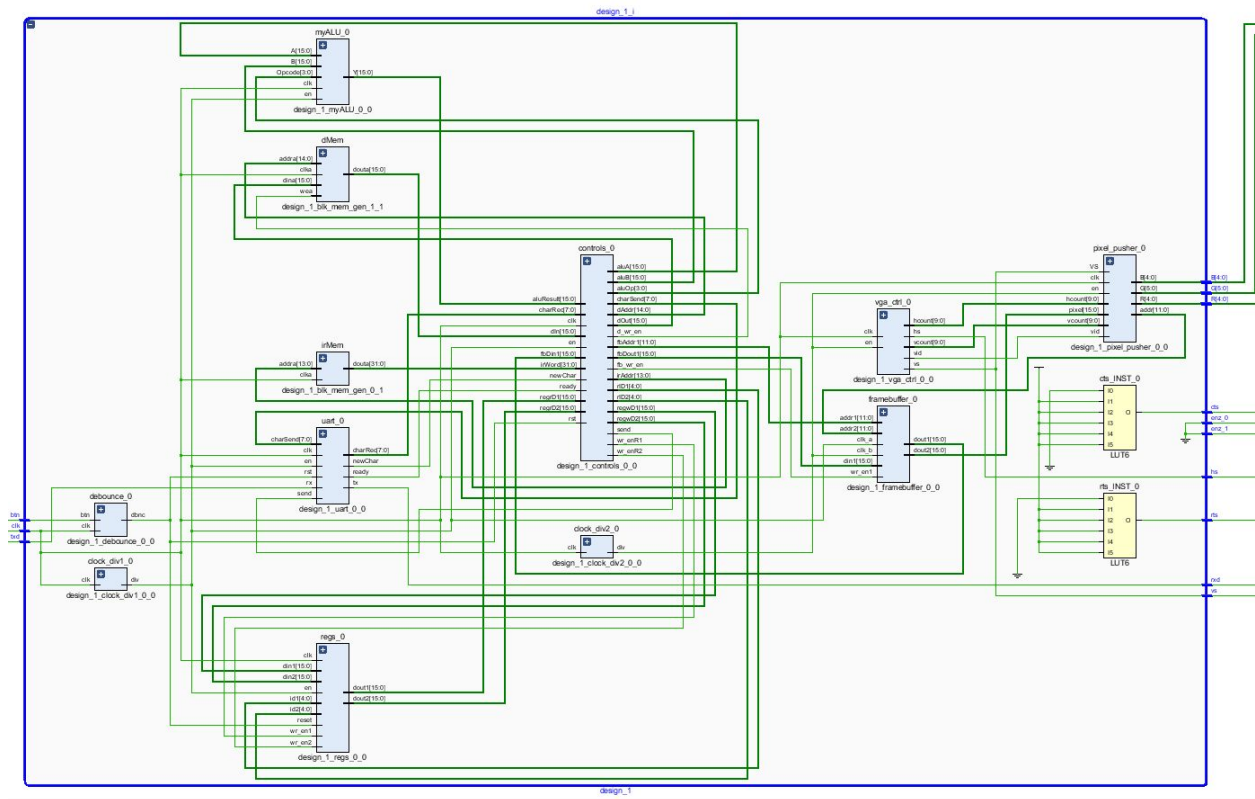


Figure 7: Synthesis Schematic of wrapper

 


Figure 8: Power Graph and Utilization Graph

## XDC File

### ZYBO\_Master.xdc

## This file is a general .xdc for the ZYBO Rev B board

## To use it in a project:

## - uncomment the lines corresponding to used pins

## - rename the used signals according to the project

##Clock signal

set\_property -dict { PACKAGE\_PIN L16 IOSTANDARD LVCMOS33 } [get\_ports { clk }]; #IO\_L11P\_T1\_SRCC\_35

Sch=sysclk

create\_clock -add -name sys\_clk\_pin -period 8.00 -waveform {0 4} [get\_ports { clk }];

##Switches

#set\_property -dict { PACKAGE\_PIN G15 IOSTANDARD LVCMOS33 } [get\_ports { sw[0] }]; #IO\_L19N\_T3\_VREF\_35  
Sch=SW0

#set\_property -dict { PACKAGE\_PIN P15 IOSTANDARD LVCMOS33 } [get\_ports { sw[1] }]; #IO\_L24P\_T3\_34 Sch=SW1

#set\_property -dict { PACKAGE\_PIN W13 IOSTANDARD LVCMOS33 } [get\_ports { sw[2] }]; #IO\_L4N\_T0\_34 Sch=SW2

#set\_property -dict { PACKAGE\_PIN T16 IOSTANDARD LVCMOS33 } [get\_ports { sw[3] }]; #IO\_L9P\_T1\_DQS\_34 Sch=SW3

##Buttons

set\_property -dict { PACKAGE\_PIN R18 IOSTANDARD LVCMOS33 } [get\_ports { btn }]; #IO\_L20N\_T3\_34 Sch=BTN0

#set\_property -dict { PACKAGE\_PIN P16 IOSTANDARD LVCMOS33 } [get\_ports { btn[1] }]; #IO\_L24N\_T3\_34 Sch=BTN1

##set\_property -dict { PACKAGE\_PIN V16 IOSTANDARD LVCMOS33 } [get\_ports { btn[2] }]; #IO\_L18P\_T2\_34 Sch=BTN2

##set\_property -dict { PACKAGE\_PIN Y16 IOSTANDARD LVCMOS33 } [get\_ports { btn[3] }]; #IO\_L7P\_T1\_34 Sch=BTN3

##LEDs

#set\_property -dict { PACKAGE\_PIN M14 IOSTANDARD LVCMOS33 } [get\_ports { led[0] }]; #IO\_L23P\_T3\_35 Sch=LED0

#set\_property -dict { PACKAGE\_PIN M15 IOSTANDARD LVCMOS33 } [get\_ports { led[1] }]; #IO\_L23N\_T3\_35 Sch=LED1

#set\_property -dict { PACKAGE\_PIN G14 IOSTANDARD LVCMOS33 } [get\_ports { led[2] }]; #IO\_0\_35=Sch=LED2

#set\_property -dict { PACKAGE\_PIN D18 IOSTANDARD LVCMOS33 } [get\_ports { led[3] }]; #IO\_L3N\_T0\_DQS\_AD1N\_35  
Sch=LED3

##I2S Audio Codec

#set\_property -dict { PACKAGE\_PIN K18 IOSTANDARD LVCMOS33 } [get\_ports ac\_bclk]; #IO\_L12N\_T1\_MRCC\_35  
Sch=AC\_BCLK

#set\_property -dict { PACKAGE\_PIN T19 IOSTANDARD LVCMOS33 } [get\_ports ac\_mclk]; #IO\_25\_34 Sch=AC\_MCLK

#set\_property -dict { PACKAGE\_PIN P18 IOSTANDARD LVCMOS33 } [get\_ports ac\_muten]; #IO\_L23N\_T3\_34

Sch=AC\_MUTEN

#set\_property -dict { PACKAGE\_PIN M17 IOSTANDARD LVCMOS33 } [get\_ports ac\_pbdat]; #IO\_L8P\_T1\_AD10P\_35

Sch=AC\_PBDAT

#set\_property -dict { PACKAGE\_PIN L17 IOSTANDARD LVCMOS33 } [get\_ports ac\_pblrc]; #IO\_L11N\_T1\_SRCC\_35

Sch=AC\_PBLRC

#set\_property -dict { PACKAGE\_PIN K17 IOSTANDARD LVCMOS33 } [get\_ports ac\_recdat]; #IO\_L12P\_T1\_MRCC\_35

Sch=AC\_RECDA

#set\_property -dict { PACKAGE\_PIN M18 IOSTANDARD LVCMOS33 } [get\_ports ac\_reclrc]; #IO\_L8N\_T1\_AD10N\_35

Sch=AC\_RECLRC

##Audio Codec/external EEPROM IIC bus

#set\_property -dict { PACKAGE\_PIN N18 IOSTANDARD LVCMOS33 } [get\_ports ac\_scl]; #IO\_L13P\_T2\_MRCC\_34

Sch=AC\_SCL

#set\_property -dict { PACKAGE\_PIN N17 IOSTANDARD LVCMOS33 } [get\_ports ac\_sda]; #IO\_L23P\_T3\_34 Sch=AC\_SDA

#### ##Additional Ethernet signals

```
#set_property -dict { PACKAGE_PIN F16  IOSTANDARD LVCMOS33 } [get_ports eth_int_b]; #IO_L6P_T0_35  
Sch=ETH_INT_B  
#set_property -dict { PACKAGE_PIN E17  IOSTANDARD LVCMOS33 } [get_ports eth_rst_b]; #IO_L3P_T0_DQS_AD1P_35  
Sch=ETH_RST_B
```

#### ##HDMI Signals

```
#set_property -dict { PACKAGE_PIN H17  IOSTANDARD TMDS_33 } [get_ports hdmi_clk_n]; #IO_L13N_T2_MRCC_35  
Sch=HDMI_CLK_N  
#set_property -dict { PACKAGE_PIN H16  IOSTANDARD TMDS_33 } [get_ports hdmi_clk_p]; #IO_L13P_T2_MRCC_35  
Sch=HDMI_CLK_P  
#set_property -dict { PACKAGE_PIN D20  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_n[0] }]; #IO_L4N_T0_35  
Sch=HDMI_D0_N  
#set_property -dict { PACKAGE_PIN D19  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_p[0] }]; #IO_L4P_T0_35  
Sch=HDMI_D0_P  
#set_property -dict { PACKAGE_PIN B20  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_n[1] }]; #IO_L1N_T0_AD0N_35  
Sch=HDMI_D1_N  
#set_property -dict { PACKAGE_PIN C20  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_p[1] }]; #IO_L1P_T0_AD0P_35  
Sch=HDMI_D1_P  
#set_property -dict { PACKAGE_PIN A20  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_n[2] }]; #IO_L2N_T0_AD8N_35  
Sch=HDMI_D2_N  
#set_property -dict { PACKAGE_PIN B19  IOSTANDARD TMDS_33 } [get_ports { hdmi_d_p[2] }]; #IO_L2P_T0_AD8P_35  
Sch=HDMI_D2_P  
#set_property -dict { PACKAGE_PIN E19  IOSTANDARD LVCMOS33 } [get_ports hdmi_cec]; #IO_L5N_T0_AD9N_35  
Sch=HDMI_CEC  
#set_property -dict { PACKAGE_PIN E18  IOSTANDARD LVCMOS33 } [get_ports hdmi_hpd]; #IO_L5P_T0_AD9P_35  
Sch=HDMI_HPD  
#set_property -dict { PACKAGE_PIN F17  IOSTANDARD LVCMOS33 } [get_ports hdmi_out_en]; #IO_L6N_T0_VREF_35  
Sch=HDMI_OUT_EN  
#set_property -dict { PACKAGE_PIN G17  IOSTANDARD LVCMOS33 } [get_ports hdmi_scl]; #IO_L16P_T2_35  
Sch=HDMI_SCL  
#set_property -dict { PACKAGE_PIN G18  IOSTANDARD LVCMOS33 } [get_ports hdmi_sda]; #IO_L16N_T2_35  
Sch=HDMI_SDA
```

#### ##Pmod Header JA (XADC)

```
#set_property -dict { PACKAGE_PIN N15  IOSTANDARD LVCMOS33 } [get_ports { ja_p[0] }]; #IO_L21P_T3_DQS_AD14P_35  
Sch=JA1_R_p  
#set_property -dict { PACKAGE_PIN L14  IOSTANDARD LVCMOS33 } [get_ports { ja_p[1] }]; #IO_L22P_T3_AD7P_35  
Sch=JA2_R_P  
#set_property -dict { PACKAGE_PIN K16  IOSTANDARD LVCMOS33 } [get_ports { ja_p[2] }]; #IO_L24P_T3_AD15P_35  
Sch=JA3_R_P  
#set_property -dict { PACKAGE_PIN K14  IOSTANDARD LVCMOS33 } [get_ports { ja_p[3] }]; #IO_L20P_T3_AD6P_35  
Sch=JA4_R_P  
#set_property -dict { PACKAGE_PIN N16  IOSTANDARD LVCMOS33 } [get_ports { ja_n[0] }];  
#IO_L21N_T3_DQS_AD14N_35 Sch=JA1_R_N  
#set_property -dict { PACKAGE_PIN L15  IOSTANDARD LVCMOS33 } [get_ports { ja_n[1] }]; #IO_L22N_T3_AD7N_35  
Sch=JA2_R_N  
#set_property -dict { PACKAGE_PIN J16  IOSTANDARD LVCMOS33 } [get_ports { ja_n[2] }]; #IO_L24N_T3_AD15N_35  
Sch=JA3_R_N  
#set_property -dict { PACKAGE_PIN J14  IOSTANDARD LVCMOS33 } [get_ports { ja_n[3] }]; #IO_L20N_T3_AD6N_35  
Sch=JA4_R_N
```

#### ##Pmod Header JB

```
set_property -dict { PACKAGE_PIN T20  IOSTANDARD LVCMOS33 } [get_ports { rts }]; #IO_L15P_T2_DQS_34 Sch=JB1_p  
set_property -dict { PACKAGE_PIN U20  IOSTANDARD LVCMOS33 } [get_ports { rxd }]; #IO_L15N_T2_DQS_34 Sch=JB1_N  
set_property -dict { PACKAGE_PIN V20  IOSTANDARD LVCMOS33 } [get_ports { txd }]; #IO_L16P_T2_34 Sch=JB2_P  
set_property -dict { PACKAGE_PIN W20  IOSTANDARD LVCMOS33 } [get_ports { cts }]; #IO_L16N_T2_34 Sch=JB2_N
```

```
#set_property -dict { PACKAGE_PIN Y18 IOSTANDARD LVCMOS33 } [get_ports { jb_p[2] }]; #IO_L17P_T2_34 Sch=JB3_P
#set_property -dict { PACKAGE_PIN Y19 IOSTANDARD LVCMOS33 } [get_ports { jb_n[2] }]; #IO_L17N_T2_34 Sch=JB3_N
#set_property -dict { PACKAGE_PIN W18 IOSTANDARD LVCMOS33 } [get_ports { jb_p[3] }]; #IO_L22P_T3_34 Sch=JB4_P
#set_property -dict { PACKAGE_PIN W19 IOSTANDARD LVCMOS33 } [get_ports { jb_n[3] }]; #IO_L22N_T3_34 Sch=JB4_N
```

#### ##Pmod Header JC

```
#set_property -dict { PACKAGE_PIN V15 IOSTANDARD LVCMOS33 } [get_ports { jc_p[0] }]; #IO_L10P_T1_34 Sch=JC1_P
#set_property -dict { PACKAGE_PIN W15 IOSTANDARD LVCMOS33 } [get_ports { jc_n[0] }]; #IO_L10N_T1_34 Sch=JC1_N
#set_property -dict { PACKAGE_PIN T11 IOSTANDARD LVCMOS33 } [get_ports { jc_p[1] }]; #IO_L1P_T0_34 Sch=JC2_P
#set_property -dict { PACKAGE_PIN T10 IOSTANDARD LVCMOS33 } [get_ports { jc_n[1] }]; #IO_L1N_T0_34 Sch=JC2_N
#set_property -dict { PACKAGE_PIN W14 IOSTANDARD LVCMOS33 } [get_ports { jc_p[2] }]; #IO_L8P_T1_34 Sch=JC3_P
#set_property -dict { PACKAGE_PIN Y14 IOSTANDARD LVCMOS33 } [get_ports { jc_n[2] }]; #IO_L8N_T1_34 Sch=JC3_N
#set_property -dict { PACKAGE_PIN T12 IOSTANDARD LVCMOS33 } [get_ports { jc_p[3] }]; #IO_L2P_T0_34 Sch=JC4_P
#set_property -dict { PACKAGE_PIN U12 IOSTANDARD LVCMOS33 } [get_ports { jc_n[3] }]; #IO_L2N_T0_34 Sch=JC4_N
```

#### ##Pmod Header JD

```
#set_property -dict { PACKAGE_PIN T14 IOSTANDARD LVCMOS33 } [get_ports { jd_p[0] }]; #IO_L5P_T0_34 Sch=JD1_P
#set_property -dict { PACKAGE_PIN T15 IOSTANDARD LVCMOS33 } [get_ports { jd_n[0] }]; #IO_L5N_T0_34 Sch=JD1_N
#set_property -dict { PACKAGE_PIN P14 IOSTANDARD LVCMOS33 } [get_ports { jd_p[1] }]; #IO_L6P_T0_34 Sch=JD2_P
#set_property -dict { PACKAGE_PIN R14 IOSTANDARD LVCMOS33 } [get_ports { jd_n[1] }]; #IO_L6N_T0_VREF_34
Sch=JD2_N
#set_property -dict { PACKAGE_PIN U14 IOSTANDARD LVCMOS33 } [get_ports { jd_p[2] }]; #IO_L11P_T1_SRCC_34
Sch=JD3_P
#set_property -dict { PACKAGE_PIN U15 IOSTANDARD LVCMOS33 } [get_ports { jd_n[2] }]; #IO_L11N_T1_SRCC_34
Sch=JD3_N
#set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports { jd_p[3] }]; #IO_L21P_T3_DQS_34
Sch=JD4_P
#set_property -dict { PACKAGE_PIN V18 IOSTANDARD LVCMOS33 } [get_ports { jd_n[3] }]; #IO_L21N_T3_DQS_34
Sch=JD4_N
```

#### ##Pmod Header JE

```
#set_property -dict { PACKAGE_PIN V12 IOSTANDARD LVCMOS33 } [get_ports { je[0] }]; #IO_L4P_T0_34 Sch=JE1
#set_property -dict { PACKAGE_PIN W16 IOSTANDARD LVCMOS33 } [get_ports { je[1] }]; #IO_L18N_T2_34 Sch=JE2
#set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { je[2] }]; #IO_25_35 Sch=JE3
#set_property -dict { PACKAGE_PIN H15 IOSTANDARD LVCMOS33 } [get_ports { je[3] }]; #IO_L19P_T3_35 Sch=JE4
#set_property -dict { PACKAGE_PIN V13 IOSTANDARD LVCMOS33 } [get_ports { je[4] }]; #IO_L3N_T0_DQS_34 Sch=JE7
#set_property -dict { PACKAGE_PIN U17 IOSTANDARD LVCMOS33 } [get_ports { je[5] }]; #IO_L9N_T1_DQS_34 Sch=JE8
#set_property -dict { PACKAGE_PIN T17 IOSTANDARD LVCMOS33 } [get_ports { je[6] }]; #IO_L20P_T3_34 Sch=JE9
#set_property -dict { PACKAGE_PIN Y17 IOSTANDARD LVCMOS33 } [get_ports { je[7] }]; #IO_L7N_T1_34 Sch=JE10
```

#### ##USB-OTG overcurrent detect pin

```
#set_property -dict { PACKAGE_PIN U13 IOSTANDARD LVCMOS33 } [get_ports otg_oc]; #IO_L3P_T0_DQS_PUDC_B_34
Sch=OTG_OC
```

#### ##VGA Connector

```
set_property -dict { PACKAGE_PIN M19 IOSTANDARD LVCMOS33 } [get_ports { R[0] }]; #IO_L7P_T1_AD2P_35
Sch=VGA_R1
set_property -dict { PACKAGE_PIN L20 IOSTANDARD LVCMOS33 } [get_ports { R[1] }]; #IO_L9N_T1_DQS_AD3N_35
Sch=VGA_R2
set_property -dict { PACKAGE_PIN J20 IOSTANDARD LVCMOS33 } [get_ports { R[2] }]; #IO_L17P_T2_AD5P_35
Sch=VGA_R3
set_property -dict { PACKAGE_PIN G20 IOSTANDARD LVCMOS33 } [get_ports { R[3] }]; #IO_L18N_T2_AD13N_35
Sch=VGA_R4
set_property -dict { PACKAGE_PIN F19 IOSTANDARD LVCMOS33 } [get_ports { R[4] }]; #IO_L15P_T2_DQS_AD12P_35
Sch=VGA_R5
set_property -dict { PACKAGE_PIN H18 IOSTANDARD LVCMOS33 } [get_ports { G[0] }]; #IO_L14N_T2_AD4N_SRCC_35
```

```

Sch=VGA_G0
set_property -dict { PACKAGE_PIN N20  IOSTANDARD LVCMOS33 } [get_ports { G[1] }]; #IO_L14P_T2_SRCC_34
Sch=VGA_G1
set_property -dict { PACKAGE_PIN L19  IOSTANDARD LVCMOS33 } [get_ports { G[2] }]; #IO_L9P_T1_DQS_AD3P_35
Sch=VGA_G2
set_property -dict { PACKAGE_PIN J19  IOSTANDARD LVCMOS33 } [get_ports { G[3] }]; #IO_L10N_T1_AD11N_35
Sch=VGA_G3
set_property -dict { PACKAGE_PIN H20  IOSTANDARD LVCMOS33 } [get_ports { G[4] }]; #IO_L17N_T2_AD5N_35
Sch=VGA_G4
set_property -dict { PACKAGE_PIN F20  IOSTANDARD LVCMOS33 } [get_ports { G[5] }]; #IO_L15N_T2_DQS_AD12N_35
Sch=VGA_G5
set_property -dict { PACKAGE_PIN P20  IOSTANDARD LVCMOS33 } [get_ports { B[0] }]; #IO_L14N_T2_SRCC_34
Sch=VGA_B1
set_property -dict { PACKAGE_PIN M20  IOSTANDARD LVCMOS33 } [get_ports { B[1] }]; #IO_L7N_T1_AD2N_35
Sch=VGA_B2
set_property -dict { PACKAGE_PIN K19  IOSTANDARD LVCMOS33 } [get_ports { B[2] }]; #IO_L10P_T1_AD11P_35
Sch=VGA_B3
set_property -dict { PACKAGE_PIN J18  IOSTANDARD LVCMOS33 } [get_ports { B[3] }]; #IO_L14P_T2_AD4P_SRCC_35
Sch=VGA_B4
set_property -dict { PACKAGE_PIN G19  IOSTANDARD LVCMOS33 } [get_ports { B[4] }]; #IO_L18P_T2_AD13P_35
Sch=VGA_B5
set_property -dict { PACKAGE_PIN P19  IOSTANDARD LVCMOS33 } [get_ports hs]; #IO_L13N_T2_MRCC_34 Sch=VGA_HS
set_property -dict { PACKAGE_PIN R19  IOSTANDARD LVCMOS33 } [get_ports vs]; #IO_0_34 Sch=VGA_VS

```

The clock signal was uncommented to use the clock. The first button was uncommented since it was used to reset. The first four pins T20, U20, V20, and W20 for the PMOD connector JB were uncommented and were assigned to rts, rxd, txd, and cts respectively. The VGA connectors were also uncommented for the R, G, B, hs, and vs signals.



## ***Discussion***

### ***Observations / Discoveries***

This one lab taught me more than an entire semester of lab sessions in other classes. I learned how to infer memory and registers. I learned how to design a controller for a processor. I learned how to use the Vivado IP integrator tool. I learned how to debug simulations with a plethora of waveforms. I feel like the more appropriate question is what didn't I learn?

### ***Questions / Follow Up***

I completely understand the importance of simulating your code. I also understand the how to use/ realize the convenience of the IP integrator tool. I am a little unsure of why I had to break up certain states of my controller into multiple parts.